

# Chapter 4 :: Hardware Description Languages

*Digital Design and Computer Architecture, 1<sup>st</sup> Edition*

David Money Harris and Sarah L. Harris

# Chapter 4 :: Topics

- **Introduction**
- **Combinational Logic**
- **Structural Modeling**
- **Sequential Logic**
- **More Combinational Logic**
- **Finite State Machines**
- **Parameterized Modules**
- **Testbenches**

# Introduction

- Hardware description language (HDL): allows designer to specify logic function only. Then a computer-aided design (CAD) tool produces or *synthesizes* the optimized gates.
- Most commercial designs built using HDLs
- Two leading HDLs:
  - **Verilog**
    - developed in 1984 by Gateway Design Automation
    - became an IEEE standard (1364) in 1995
  - **VHDL**
    - Developed in 1981 by the Department of Defense
    - Became an IEEE standard (1076) in 1987

# HDL to Gates

- **Simulation**

- Input values are applied to the circuit
- Outputs checked for correctness
- Millions of dollars saved by debugging in simulation instead of hardware


- **Synthesis**

- Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)

## IMPORTANT:

When describing circuits using an HDL, it's critical to think of the **hardware** the code should produce.

# Verilog Modules

 

## Two types of Modules:

- Behavioral: describe what a module does
- Structural: describe how a module is built from simpler modules

# Behavioral Verilog Example


## Verilog:

```
module example(input  a, b, c,  
               output y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b &  c;  
endmodule
```

# Behavioral Verilog Simulation

## Verilog:

```
module example(input  a, b, c,  
               output y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b &  c;  
endmodule
```

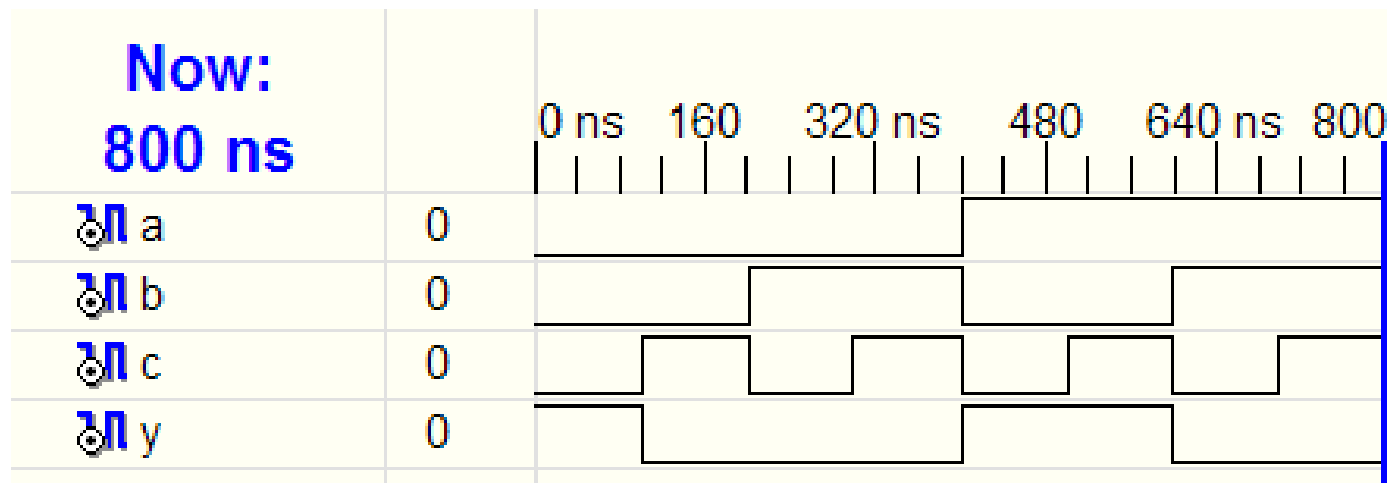


# Behavioral Verilog Synthesis

## Verilog:

```
module example(input  a, b, c,  
               output y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b &  c;  
endmodule
```

## Synthesis:

 



# Verilog Syntax

- Case sensitive
  - Example: `reset` and `Reset` are not the same signal.
- No names that start with numbers
  - Example: `2mux` is an invalid name.
- Whitespace ignored
- Comments:
  - `//` single line comment
  - `/*` multiline  
comment `*/`

# Structural Modeling - Hierarchy


```
module and3(input  a, b, c,  
            output y);  
    assign y = a & b & c;  
endmodule
```

```
module inv(input  a,  
            output y);  
    assign y = ~a;  
endmodule
```

```
module nand3(input  a, b, c  
             output y);  
    wire n1;                                // internal signal  
  
    and3 andgate(a, b, c, n1);              // instance of and3  
    inv  inverter(n1, y);                   // instance of inverter  
endmodule
```

# Bitwise Operators

```
module gates(input [3:0] a, b,  
            output [3:0] y1, y2, y3, y4, y5);  
    /* Five different two-input logic  
       gates acting on 4 bit busses */  
    assign y1 = a & b; // AND  
    assign y2 = a | b; // OR  
    assign y3 = a ^ b; // XOR  
    assign y4 = ~(a & b); // NAND  
    assign y5 = ~(a | b); // NOR  
endmodule
```

 


// single line comment

/\* ... \*/ multiline comment

 
# Reduction Operators

```
module and8(input [7:0] a,  
            output y);  
    assign y = &a;  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    // a[3] & a[2] & a[1] & a[0];  
endmodule
```


 
# Conditional Assignment


```
module mux2(input [3:0] d0, d1,  
            input      s,  
            output [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```



? : is also called a *ternary operator* because it operates on 3 inputs:  $s$ ,  $d1$ , and  $d0$ .

# Internal Variables

```
module fulladder(input a, b, cin, output s, cout);  
  wire p, g;          // internal nodes  
  
  assign p = a ^ b;  
  assign g = a & b;  
  
  assign s = p ^ cin;  
  assign cout = g | (p & cin);  
endmodule
```

 

# Precedence

Defines the order of operations

Highest

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
?:	ternary operator

Lowest



# Numbers

Format: N'Bvalue

N = number of bits, B = base

N'B is optional but recommended (default is decimal)

Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	Unsized	decimal	42	00...0101010



# Bit Manipulations: Example 1

```
assign y = {a[2:1], {3{b[0]}}, a[0], 6'b100_010};
```

**// if y is a 12-bit signal, the above statement produces:**

```
y = a[2] a[1] b[0] b[0] b[0] a[0] 1 0 0 0 1 0
```


// underscores (\_) are used for formatting only to make it easier to read. Verilog ignores them.

# Bit Manipulations: Example 2

## Verilog:

```
module mux2_8(input [7:0] d0, d1,  
             input      s,  
             output [7:0] y);  
  
    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);  
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);  
endmodule
```

## Synthesis:

 


# Z: Floating Output

## Verilog:


```
module tristate(input [3:0] a,  
               input      en,  
               output [3:0] y);  
    assign y = en ? a : 4'bz;  
endmodule
```

## Synthesis:

 


# Delays

```
module example(input a, b, c,  
              output y);  
    wire ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} = ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 

# Delays

```
module example(input a, b, c,  
               output y);  
    wire ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
            ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 

# Sequential Logic

- Verilog uses certain idioms to describe latches, flip-flops and FSMs
- Other coding styles may simulate correctly but produce incorrect hardware

# Always Statement

## General Structure:

```
always @ (sensitivity list)
    statement;
```

Whenever the event in the sensitivity list occurs, the statement is executed

# D Flip-Flop

```
module flop(input          clk,  
           input    [3:0] d,  
           output reg [3:0] q);  
  
  always @ (posedge clk)  
    q <= d;                // pronounced "q gets d"  
  
endmodule
```



Any signal assigned in an `always` statement must be declared `reg`. In this case `q` is declared as `reg`

**Beware:** A variable declared `reg` is not necessarily a registered output. We will show examples of this later.




# Resettable D Flip-Flop

```
module flopr(input          clk,  
            input          reset,  
            input  [3:0]  d,  
            output reg [3:0] q);
```


```
// synchronous reset  
always @ (posedge clk)  
    if (reset) q <= 4'b0;  
    else      q <= d;
```

```
endmodule
```

 

 
# Resettable D Flip-Flop

```
module flopr(input          clk,  
            input          reset,  
            input    [3:0] d,  
            output reg [3:0] q);  
  
    // asynchronous reset  
    always @ (posedge clk, posedge reset)  
        if (reset) q <= 4'b0;  
        else      q <= d;  
  
endmodule
```



 
# D Flip-Flop with Enable

```
module flopren(input          clk,  
              input          reset,  
              input          en,  
              input [3:0] d,  
              output reg [3:0] q);  
  
// asynchronous reset and enable  
always @ (posedge clk, posedge reset)  
    if (reset) q <= 4'b0;  
    else if (en) q <= d;  
  
endmodule
```


 
# Latch

```
module latch(input          clk,  
             input    [3:0] d,  
             output reg [3:0] q);  
  
    always @ (clk, d)  
        if (clk) q <= d;  
  
endmodule
```



**Warning:** We won't use latches in this course, but you might write code that inadvertently implies a latch. So if your synthesized hardware has latches in it, this indicates an error.

# Other Behavioral Statements

- Statements that must be inside `always` statements:
  - `if / else`
  - `case, casez`
- **Reminder:** Variables assigned in an `always` statement must be declared as `reg` (even if they're not actually registered!)

# Combinational Logic using always

```
// combinational logic using an always statement
module gates(input      [3:0] a, b,
              output reg [3:0] y1, y2, y3, y4, y5);
  always @(*)          // need begin/end because there is
    begin              // more than one statement in always
      y1 = a & b;      // AND
      y2 = a | b;      // OR
      y3 = a ^ b;      // XOR
      y4 = ~(a & b);   // NAND
      y5 = ~(a | b);   // NOR
    end
endmodule
```

This hardware could be described with assign statements using fewer lines of code, so it's better to use assign statements in this case.

# Combinational Logic using case

```
module sevenseg(input      [3:0] data,  
                output reg [6:0] segments);  
  always @(*)  
    case (data)  
      //                abc_defg  
      0: segments = 7'b111_1110;  
      1: segments = 7'b011_0000;  
      2: segments = 7'b110_1101;  
      3: segments = 7'b111_1001;  
      4: segments = 7'b011_0011;  
      5: segments = 7'b101_1011;  
      6: segments = 7'b101_1111;  
      7: segments = 7'b111_0000;  
      8: segments = 7'b111_1111;  
      9: segments = 7'b111_1011;  
      default: segments = 7'b000_0000; // required  
    endcase  
endmodule
```


# Combinational Logic using case

- In order for a `case` statement to imply combinational logic, all possible input combinations must be described by the HDL.
- Remember to use a **default** statement when necessary.


 
# Combinational Logic using casez

```
module priority_casez(input [3:0] a,  
                    output reg [3:0] y);  
  
    always @(*)  
        casez(a)  
            4'b1???: y = 4'b1000; // ? = don't care  
            4'b01??: y = 4'b0100;  
            4'b001?: y = 4'b0010;  
            4'b0001: y = 4'b0001;  
            default: y = 4'b0000;  
        endcase  
  
endmodule
```




# Blocking vs. Nonblocking Assignments

- `<=` is a “nonblocking assignment”
  - Occurs simultaneously with others
- `=` is a “blocking assignment”
  - Occurs in the order it appears in the file


```
// Good synchronizer using
// nonblocking assignments
module syncgood(input      clk,
                input      d,
                output reg q);

     reg n1;
    always @(posedge clk)
    begin
        n1 <= d; // nonblocking
        q  <= n1; // nonblocking
    end
endmodule
```



```
// Bad synchronizer using
// blocking assignments
module syncbad(input      clk,
                input      d,
                output reg q);

     reg n1;
    always @(posedge clk)
    begin
        n1 = d; // blocking
        q  = n1; // blocking
    end
endmodule
```



# Rules for Signal Assignment

- Use `always @ (posedge clk)` and nonblocking assignments (`<=`) to model synchronous sequential logic

```
always @ (posedge clk)
    q <= d; // nonblocking
```

- Use continuous assignments (`assign ...`) to model simple combinational logic.


```
assign y = a & b;
```

- Use `always @ (*)` and blocking assignments (`=`) to model more complicated combinational logic where the `always` statement is helpful.
- Do not make assignments to the same signal in more than one `always` statement or continuous assignment statement.



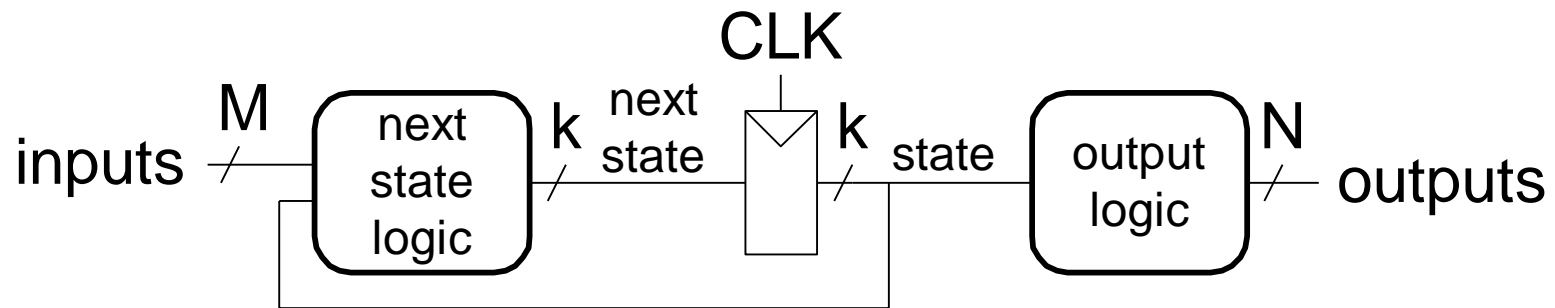
# Finite State Machines (FSMs)

- Three blocks:
  - next state logic
  - state register
  - output logic



# FSM Example: Divide by 3

 

The double circle indicates the reset state

# FSM in Verilog

```
module divideby3FSM (input  clk,
                    input  reset,
                    output q);
    reg  [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;

    // state register
    always @ (posedge clk, posedge reset)
        if (reset) state <= S0;
        else      state <= nextstate;
    // next state logic
    always @ (*)
        case (state)
            S0:    nextstate = S1;
            S1:    nextstate = S2;
            S2:    nextstate = S0;
            default: nextstate = S0;
        endcase
    // output logic
    assign q = (state == S0);
endmodule
```

# Parameterized Modules

## 2:1 mux:

```
module mux2
    #(parameter width = 8) // name and default value
    (input [width-1:0] d0, d1,
     input          s,
     output [width-1:0] y);
    assign y = s ? d1 : d0;
endmodule
```

## Instance with 8-bit bus width (uses default):

```
mux2 mux1(d0, d1, s, out);
```

## Instance with 12-bit bus width:

```
mux2 #(12) lowmux(d0, d1, s, out);
```

# Testbenches

- HDL code written to test another HDL module, the *device under test* (dut), also called the *unit under test* (uut)
- Not synthesizable
- Types of testbenches:
  - Simple testbench
  - Self-checking testbench
  - Self-checking testbench with testvectors



# Example

Write Verilog code to implement the following function in hardware:

$$y = \overline{bc} + a\overline{b}$$

Name the module `sillyfunction`

# Example

Write Verilog code to implement the following function in hardware:

$$y = \overline{bc} + a\overline{b}$$

Name the module `sillyfunction`

## Verilog

```
module sillyfunction(input  a, b, c,
                      output y);
    assign y = ~b & ~c | a & ~b;
endmodule
```

# Week 4

# Simple Testbench

```
module testbench1();  
    reg a, b, c;  
    wire y;  
    // instantiate device under test  
    sillyfunction dut(a, b, c, y);  
    // apply inputs one at a time  
    initial begin  
        a = 0; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
        a = 1; b = 0; c = 0; #10;  
        c = 1; #10;  
        b = 1; c = 0; #10;  
        c = 1; #10;  
    end  
endmodule
```

# Self-checking Testbench


```
module testbench2();
    reg a, b, c;
    wire y;
    // instantiate device under test
    sillyfunction dut(a, b, c, y);
    // apply inputs one at a time
    // checking results
    initial begin
        a = 0; b = 0; c = 0; #10;
        if (y !== 1) $display("000 failed.");
        c = 1; #10;
        if (y !== 0) $display("001 failed.");
        b = 1; c = 0; #10;
        if (y !== 0) $display("010 failed.");
        c = 1; #10;
        if (y !== 0) $display("011 failed.");
        a = 1; b = 0; c = 0; #10;
        if (y !== 1) $display("100 failed.");
        c = 1; #10;
        if (y !== 1) $display("101 failed.");
        b = 1; c = 0; #10;
        if (y !== 0) $display("110 failed.");
        c = 1; #10;
        if (y !== 0) $display("111 failed.");
    end
endmodule
```

# Testbench with Testvectors

- Write testvector file: inputs and expected outputs
- Testbench:
  1. Generate clock for assigning inputs, reading outputs
  2. Read testvectors file into array
  3. Assign inputs, expected outputs
  4. Compare outputs to expected outputs and report errors
 
# Testbench with Testvectors

- Testbench clock is used to assign inputs (on the rising edge) and compare outputs with expected outputs (on the falling edge).



- The testbench clock may also be used as the clock source for synchronous sequential circuits.

# Testvectors File

**File:** `example.tv` - contains vectors of `abc_yexpected`

`000_1`

`001_0`

`010_0`

`011_0`

`100_1`

`101_1`

`110_0`

`111_0`



# Testbench: 1. Generate Clock

```
module testbench3();
    reg            clk, reset;
    reg            a, b, c, yexpected;
    wire           y;
    reg [31:0]     vectornum, errors;    // bookkeeping variables
    reg [3:0]      testvectors[10000:0]; // array of testvectors

    // instantiate device under test
    sillyfunction dut(a, b, c, y);

    // generate clock
    always         // no sensitivity list, so it always executes
        begin
            clk = 1; #5; clk = 0; #5;
        end
end
```

## 2. Read Testvectors into Array

```
// at start of test, load vectors  
// and pulse reset
```

```
initial  
begin  
    $readmemb("example.tv", testvectors);  
    vectornum = 0; errors = 0;  
    reset = 1; #27; reset = 0;  
end
```

```
// Note: $readmemb reads testvector files written in  
// hexadecimal
```

### 3. Assign Inputs and Expected Outputs

```
// apply test vectors on rising edge of clk
always @(posedge clk)
  begin
    #1; {a, b, c, yexpected} = testvectors[vectornum];
  end
```

## 4. Compare Outputs with Expected Outputs

```
// check results on falling edge of clk
always @(negedge clk)
  if (~reset) begin // skip during reset
    if (y !== yexpected) begin
      $display("Error: inputs = %b", {a, b, c});
      $display("  outputs = %b (%b expected)", y, yexpected);
      errors = errors + 1;
    end
  end

// Note: to print in hexadecimal, use %h. For example,
//      $display("Error: inputs = %h", {a, b, c});
```

## 4. Compare Outputs with Expected Outputs

```
// increment array index and read next testvector
vectornum = vectornum + 1;
if (testvectors[vectornum] === 4'bx) begin
    $display("%d tests completed with %d errors",
            vectornum, errors);
    $finish;
end
end
endmodule
```

```
// Note: === and !== can compare values that are
// 1, 0, x, or z.
```